



EECT 7325 VLSI DESIGN

256 WORD DUAL SRAM DESIGN

Area of Memory cell	$3.42\mu\text{m} \times 2.38 \mu\text{m} = 8.1396 \text{ squm}$	
Aspect Ratio of Memory cell	1.436	
Memory array area	$102.860 \times 151.210 = 15553.4606 \text{ squm}$	
Memory area per bit	6.459	
Total Memory area	$213.520 \times 170.231 = 36347.723 \text{ squm}$	
Total Memory area per bit	17.74	
Aspect Ratio of total memory	0.797	
Worst case Write time	For '0' = 451 ps	For '1' = 467 ps
Worst case Read time	For '0' = 20.6 ns	For '1' = 1.59 ns

TABLE OF CONTENTS

1. INTRODUCTION	4
1.1 Introduction to SRAM	4
1.2 SRAM Architecture	4
1.3 8T (Eight transistor Memory Cell).....	4
1.4 Memory array	6
2. ROW DECODERS	7
2.1 Pre Decoded Style row decoder and Sizing of the transistors in the Row decoder	7
2.2 Transistor sizing	8
3. COLUMN DECODERS	9
3.1 Sizing of the transistors in the column decoder	9
3.2 Transistor sizing	9
4. SENSE AMPLIFIERS	11
5. WRITE BUFFERS	12
6. AUXILLARY CIRCUITS	13
6.1 Pass transistors	13
6.2 Pre-charger	14
6.3 Clock Buffer.....	14
6.4 Input Drivers for address bits and address enable addr_en, read enable read_en	16
7. DRC AND LVS OF SRAM DESIGN	20
8. TIMING ANALYSIS	22
8.1 HSPICE code	Error! Bookmark not defined.
8.2 Testing the correct functionality	Error! Bookmark not defined.
8.3 Worst Case Write Time for Zero and One.....	25
8.4 Worst Case Read Time for Zero and One.....	25
8.5 Operating Frequency.....	26
9. RESULTS AND CONCLUSIONS.....	27

LIST OF FIGURES

Figure 1 Memory Cell Schematic	5
Figure 2 Memory Cell Layout.....	5
Figure 3 Memory Array Layout.....	Error! Bookmark not defined.
Figure 4 Schematic of Row Decoder (Single Row).....	Error! Bookmark not defined.
Figure 5 Layout of Row decoder (Single Row).....	Error! Bookmark not defined.
Figure 6 Schematic of Column decoder.....	Error! Bookmark not defined.
Figure 7 Layout of Column decoder.....	Error! Bookmark not defined.
Figure 8 Schematic of Memory Cell Array.....	11
Figure 9 Layout of Memory Cell Array	11
Figure 10 Schematic of Sense Amplifier	12
Figure 11 Layout of Sense Amplifier	12
Figure 12 Schematic of Write Buffers	13
Figure 13 Layout of write buffer.....	13
Figure 14 Schematic of Pass Transistor	14
Figure 15 Layout of Pass Transistor	14
Figure 16 Layout of Pre- charger circuit.....	15
Figure 17 Schematic of Pre- Charger Circuit.....	Error! Bookmark not defined.
Figure 18 Schematic of Clock buffer.....	Error! Bookmark not defined.
Figure 19 Layout of Clock buffer	Error! Bookmark not defined.
Figure 20 Schematic of Input Drivers for address bits and address enable ...	Error! Bookmark not defined.
Figure 21 Layout of Input Drivers for address bits and address enable.....	Error! Bookmark not defined.
Figure 22 Schematic of Input Drivers for address bits and read enables	20
Figure 23 Layout of Input Drivers for address bits and read enables.....	20
Figure 24 DRC Report	21
Figure 25 LVS Report.....	21
Figure 26 Functionality check of write 10101010	25
Figure 27 Functionality check of read 10101010.....	24
Figure 28 Worst Case Write Time for Zero and One.....	25
Figure 29 Worst Case Read Time for Zero and One.....	25
Figure 30 Operating Frequency.....	26

1. INTRODUCTION

1.1 Introduction to SRAM

A 256 word Dual SRAM (word size is 8 bits) is designed using 130nm CMOS technology. Worst case read and write times are calculated for the output load as 25fF.

An SRAM cell consists of the following blocks:

- (a) 8T (Eight transistor) Memory cell
- (b) Row decoder
- (c) Column decoder
- (d) Precharger and clock
- (d) Sense amplifier
- (e) Write driver

1.2 SRAM Architecture

The SRAM array with the given specifications is made up of 256 words, which is split into 8 words per row, with 32 rows depending on the aspect ratio. Each word is made up of 8 bits. There are 32 word lines, hence we have a 5x32 row decoder.

Number of columns= 64

Number of rows =32

1.3 8T (Eight transistor Memory Cell)

The 8T Memory cell employs two more transistors to access read bitline. The additional two transistors are added to reduce leakage current.

The main purpose of 8T cell, for separate write/read and word signal lines as shown in the figure 1, to separate data storage and data output lines.

Write access to cell occurs through the write access transistors and from write bitlines, wbl and wblb. Read access to the cell is through read access transistors and controlled by the read wordline, rw1. Read bitline, rbl is precharged prior to the read access. The wordline for read is distinct from the write wordline.

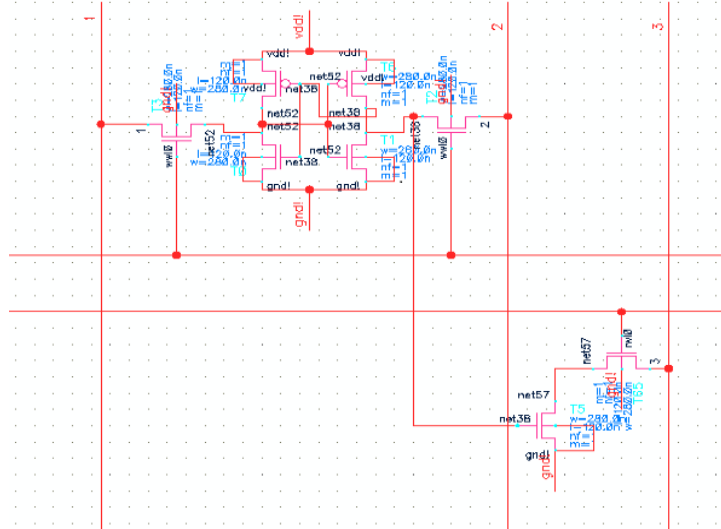


Fig.1 Memory cell schematic

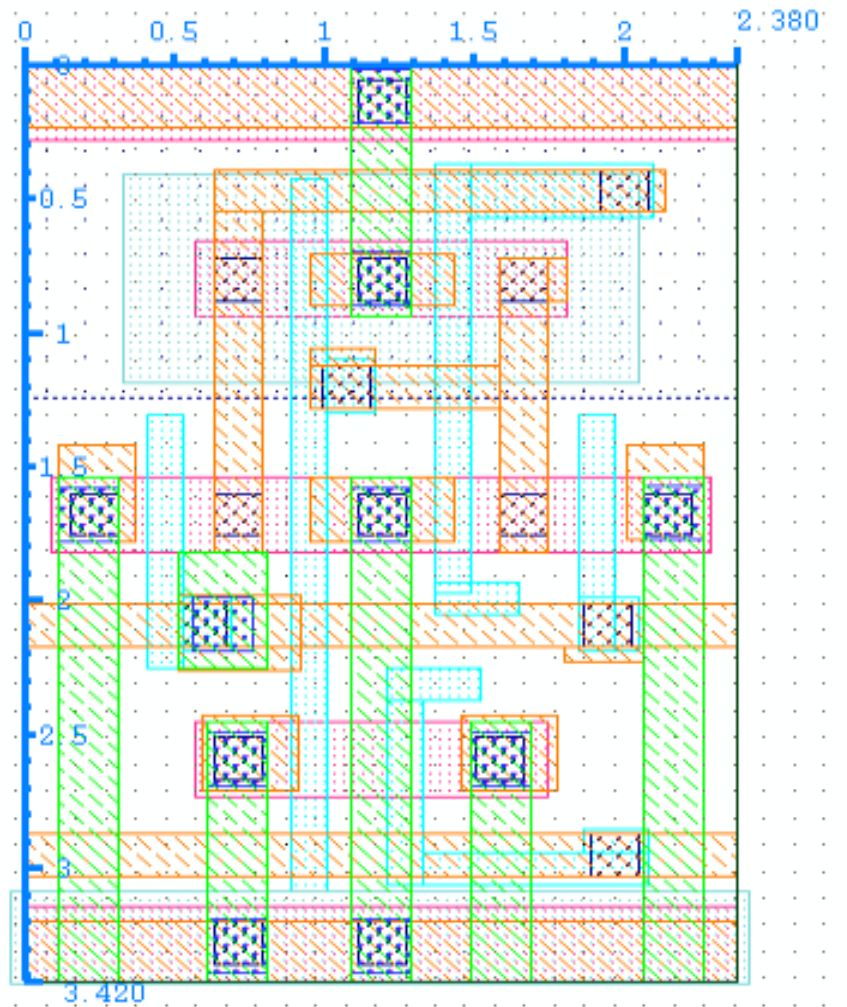


Fig.2 Memory Cell Layout

1.4 Memory array:

The Memory Array consists of 2048 memory cells, placed in 32 rows and 64 columns.

Memory cell:

Width of the cell = 2.38 μm

Height of the cell = 3.42 μm

Area of 8T cell = 8.1396 sq μm

Aspect Ratio = 1.4369

 


Fig.3 Memory Array Layout

Width = 102.860 μm

Height = 151.210 μm

Area = 102.860 x 151.210 = 15553.4606 sq μm

Area per bit = 6.459 sq μm /bit

2. ROW DECODERS

The row decoder will activate the wordlines, wwl in our memory cell. In this project, we used a pre decoded row decoder. Two row decoders are used, one for read and the other for write.

2.1 Pre Decoded Style row decoder and Sizing of the transistors in the Row decoder

We are having 5 inputs to the row decoder. The design has been implemented by using two 3 input nand gates, one 2 input nor gate and an inverter. By using the necessary information from the single 8T cell, and by using logical effort, we determined the optimum number of stages and then the sizes of the transistors used in the row decoder in the following way.

$$\begin{aligned}C_{Poly} &= 32 \times 2fF \times 2 \times 0.28 = 35.84 \text{ fF} \\C_{wire} &= 32 \times 2.38 \times 0.2fF = 15.232 \text{ fF} \\C_{load} &= C_{poly} + C_{wire} = 51.072 \text{ fF} = 25.5\mu m\end{aligned}$$

By simulating in Hspice, the Cload was changed to 53.5fF (26.75um)

G for two 3-input NAND gate, inverter and 2-input NOR gate = 125/27

B= 32

H=26.75

From $F = GBH = 3962.96$

$N = \log_{3.6} F = 6$ (Considered)

$$\hat{f} = F^{\frac{1}{N}} = 3.978$$

2.2 Transistor sizing

Inverter 1(rightmost) = 6.724 um

NAND3= 2.817 um

NOR2= 4.721 um

NAND3= 1.978 um

Inverter4= 1.988 um

The inputs to the row decoder are addr0, addr1, addr2, addr3, addr4 and addr0b, addr1b, addr2b, addr3b, addr4b. The outputs of row decoders are fed to pass transistors to activate the rows.

3. COLUMN DECODERS

The column decoder will activate the pass transistors, which drives the word bitlines, wbl and wblb. Two column decoders are used, one for read and the other for write.

3.1 Sizing of the transistors in the column decoder

Calculations:

$$C_{poly} = 2 \times 2fF \times 8 = 32fF$$

$$C_{wire} = (2.38 \mu m \times 32 \times 2) + (8 \times 0.16 \times 15) \times 0.2fF = 34.304 fF$$

$$C_{load} = C_{poly} + C_{wire} = 66.304 fF = 33.152 \mu m$$

$$F = GBH = 1064.38$$

$$N = 6 \text{ Stages}$$

$$\hat{f} = F^{\frac{1}{N}} = 3.195$$

3.2 Transistor sizing

$$\text{Inverter 1 (Right most)} = 10.410 \mu m$$

$$\text{Inverter 2} = 6.516 \mu m$$

$$\text{Inverter 3} = 2.039 \mu m$$

$$\text{NAND4} = 1.276 \mu m$$

$$\text{Inverter 5} = 1.59$$

The outputs of the column decoders will be given as inputs to the pass transistors.

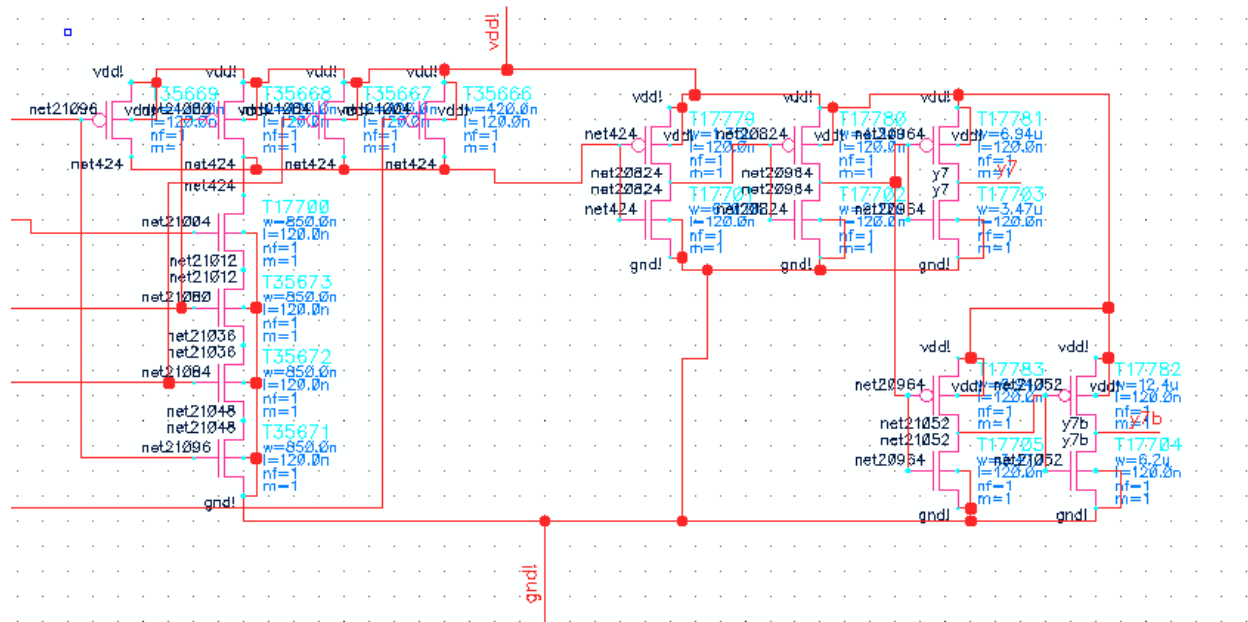


Fig.6 Schematic of Column decoder

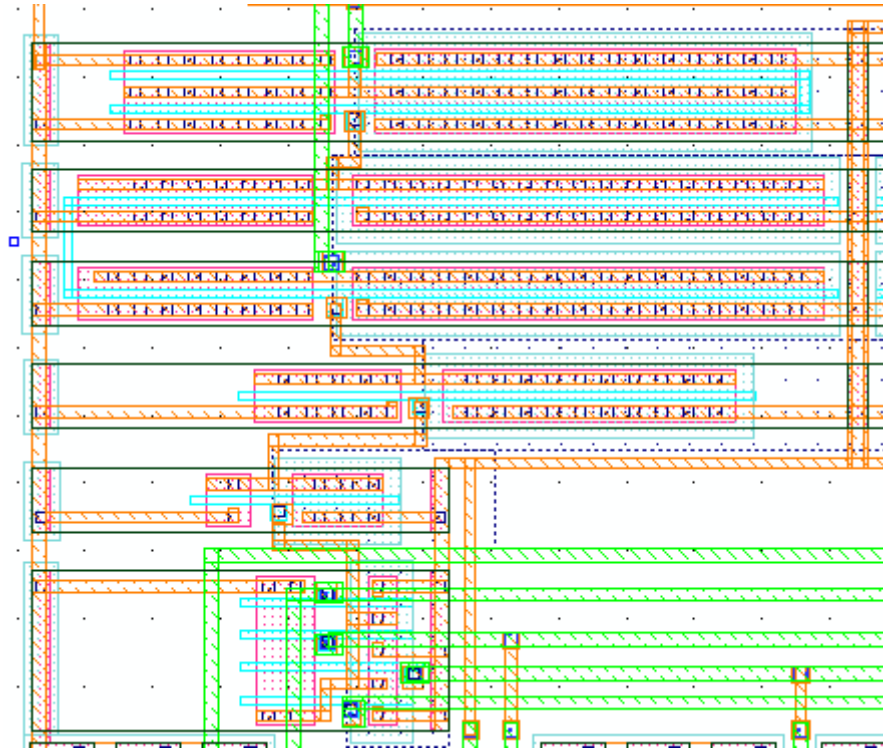


Fig.7 Layout of Column Decoder

4. SENSE AMPLIFIER

We used a Differential Amplifier on the bit lines to sense the voltage differences between wbl and wblb. The values are passed through pass transistors and are sensed by the sense amplifier. **We used transistors of sizes 0.84 μm for PMOS and 0.28 μm for NMOS in the circuit.** We have given a read bitline, rbl as input to the bottom most NMOS of the circuit.

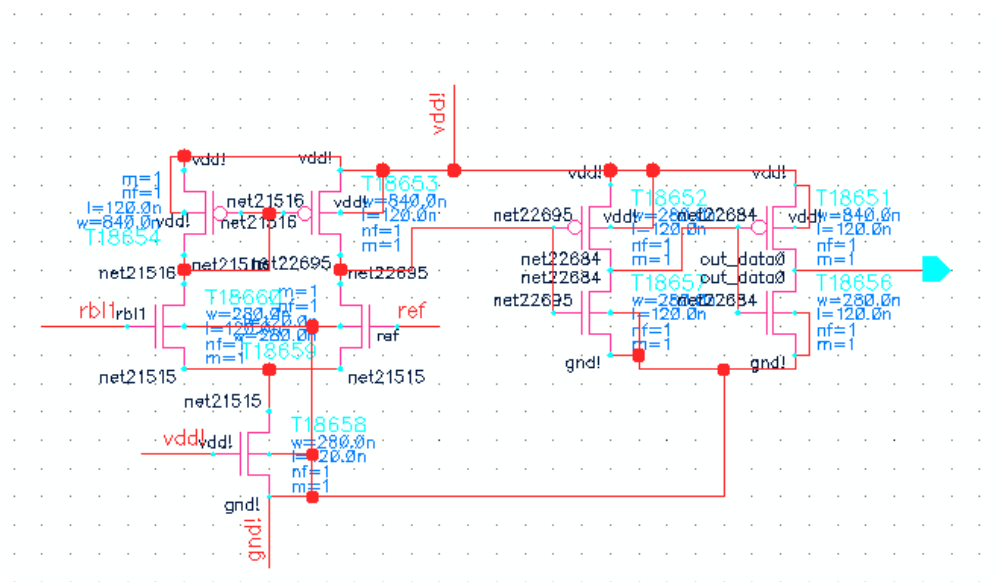


Fig.8 Schematic of Sense Amplifier

 


Fig.9 Layout of Sense Amplifier

5. WRITE BUFFERS

We used 2 Tri-state Transistors of sizes 6 um for PMOS and 6 um for NMOS.

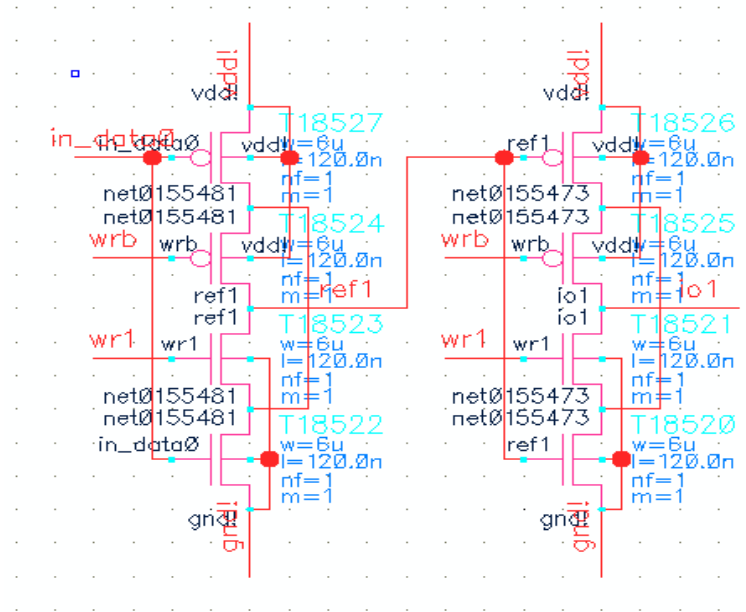


Fig.10 Schematic of Write Buffer



Fig.11 Layout of Write Buffer

6. AUXILIARY CIRCUITS

6.1 Pass transistors

The size of PMOS and NMOS is 1 μm .

 


Fig.12 Schematic of Pass Transistor

 


Fig.13 Layout of Pass Transistor

6.2 Pre-charger

The pre charger is used for bit line, wbl and wblb conditioning, which means to pre charge the bit line to V_{DD} before the next read or writes operation. Two PMOS transistors size is taken as $2\mu\text{m}$ for good conditioning of bit line and bit line bars.

 


Fig.14 Schematic of Pre-charger

 


Fig.15 Layout of Pre-charger

6.3 Clock Buffer

A clock buffer is used to provide the clock input to the pre chargers. Input to the clock is defined in the Hspice code. At the pre charge state all the bit lines will be going to V_{DD} .

Calculations:

$$C_{\text{poly}} = 2 \times 2\text{fF} \times 3 \times 64 = 768 \text{ fF}$$

$$C_{\text{wire}} = 0.2\text{fF} \times 152.27 = 30.454\text{ fF}$$

$$C_{\text{load}} = 798.54\text{ fF} = 399.232\text{ um}$$

$$F = GBH = 399.232\text{ um}$$

$$N = 5$$

$$\hat{f} = F^{\frac{1}{N}} = 3.313$$

Transistor sizes:

Inverter 1 (Right most) = 120.50 um

Inverter 2 = 36.37 um

Inverter 3 = 10.978 um

Inverter 4 = 3.313 um

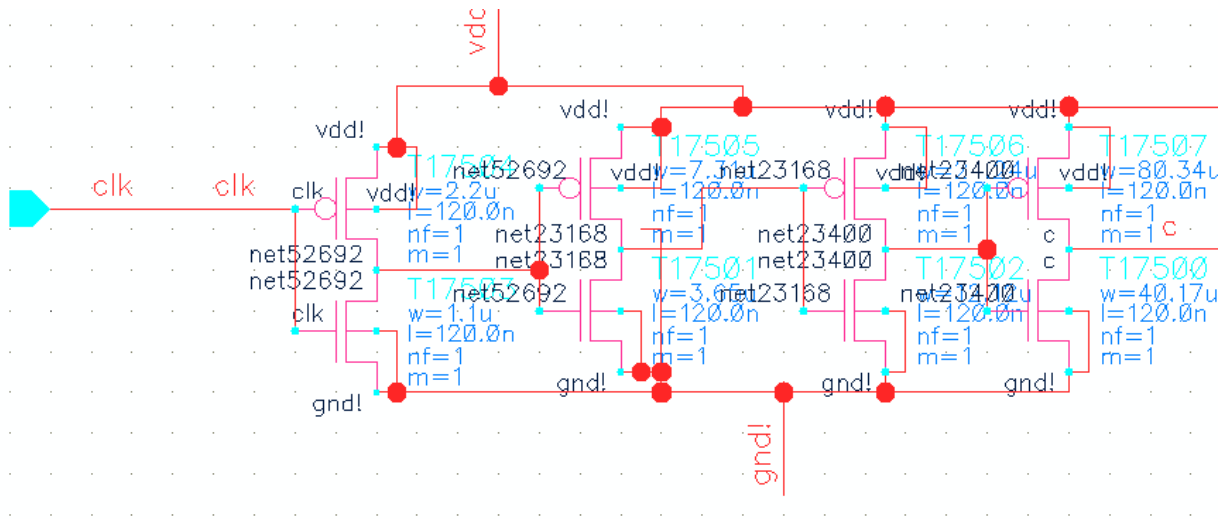


Fig.16 Schematic of Clock Buffer

 


Fig.17 Layout of Clock Buffer

6.4 Input Drivers for address bits and address enable addr_en, read enable read_en:

Sizing for address bits: addr0, addr1, addr2, addr3, addr4

Cload = 1.978 um

$$\hat{f} = F^{\frac{1}{N}} = 3.978$$

$$\text{sqrt } \hat{f} = 1.994$$

Inverter 1 (Rightmost) = 1.988 um

Inverter 2 = 1.988 um

Inverter 3 = 3.967 um

Sizing for address enable: addr_en1 and addr_en2

Clload = 4.721 uM

$$\hat{f} = F \frac{1}{N} = 3.355$$

Inverter 1 (Rightmost) = 11.257 uM

Inverter 2 = 3.355 uM

Inverter 3 = 3.967 uM

$$\text{sqrt } \hat{f} = 1.831$$

Inverter 1 (Rightmost) = 20.626 uM

Inverter 2 = 11.265 uM

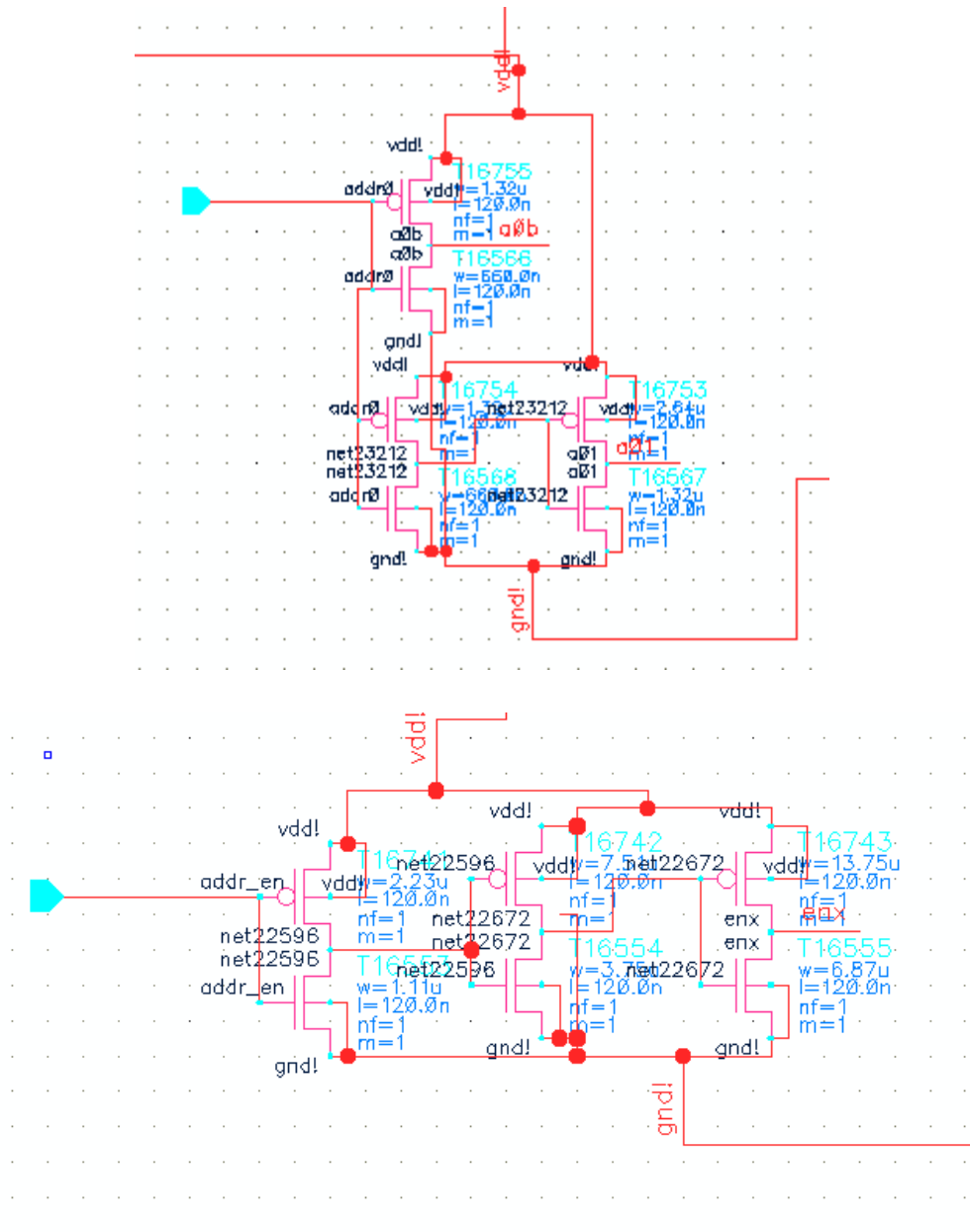


Fig.18 Schematic for Address bits and Address enable

 


Fig.19 Layout for Address bits and Address enable

Sizing for address bits: addr5, addr6, addr7

Clload = 1.276 um

$$\hat{f} = F \frac{1}{N} = 3.195$$

$$\text{sqrt } \hat{f} = 1.787$$

Inverter 1 (Rightmost) = 1.59 um

Inverter 2 = 1.59 um

Inverter 3 = 0.714 um

Sizing for read enable: read_en1, read_en2

Clload = 1.276 um

$$\hat{f} = F \frac{1}{N} = 2.169$$

Inverter 1 (Rightmost) = 4.706 um

Inverter 2 = 2.169 um

 


Fig.20 Schematic of Address bits and Read enables

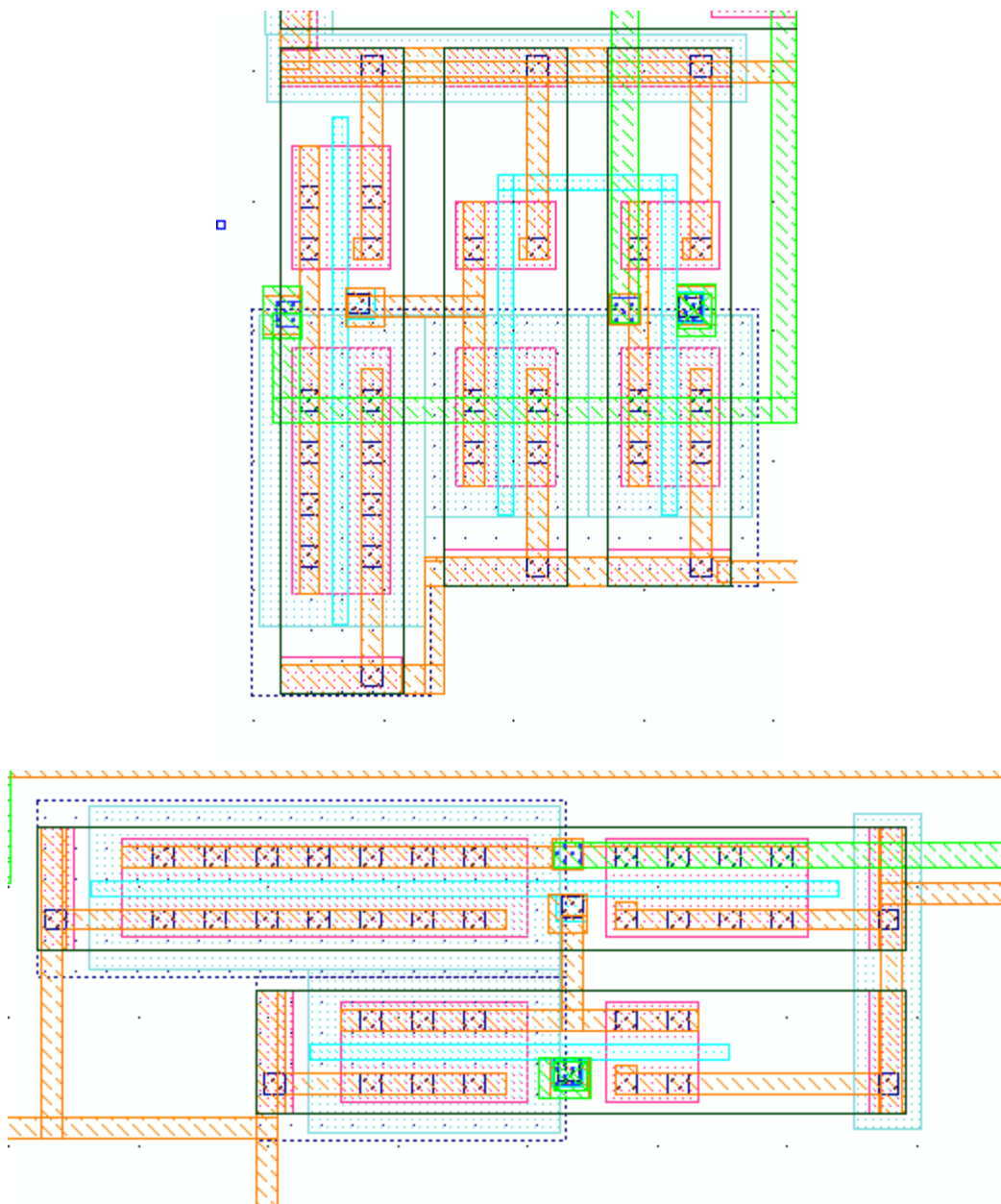


Fig.21 Layout of Address bits and Read enables

7. DRC AND LVS OF SRAM DESIGN

 


Fig.22 Schematic of Memory Cell Array

 


Fig.23 Layout of Memory Cell Array

Total Area = (213.520 um x 170.231 um) = 36347.723 sq um

Total area per bit = 17.747sq um

Aspect ratio = 0.797

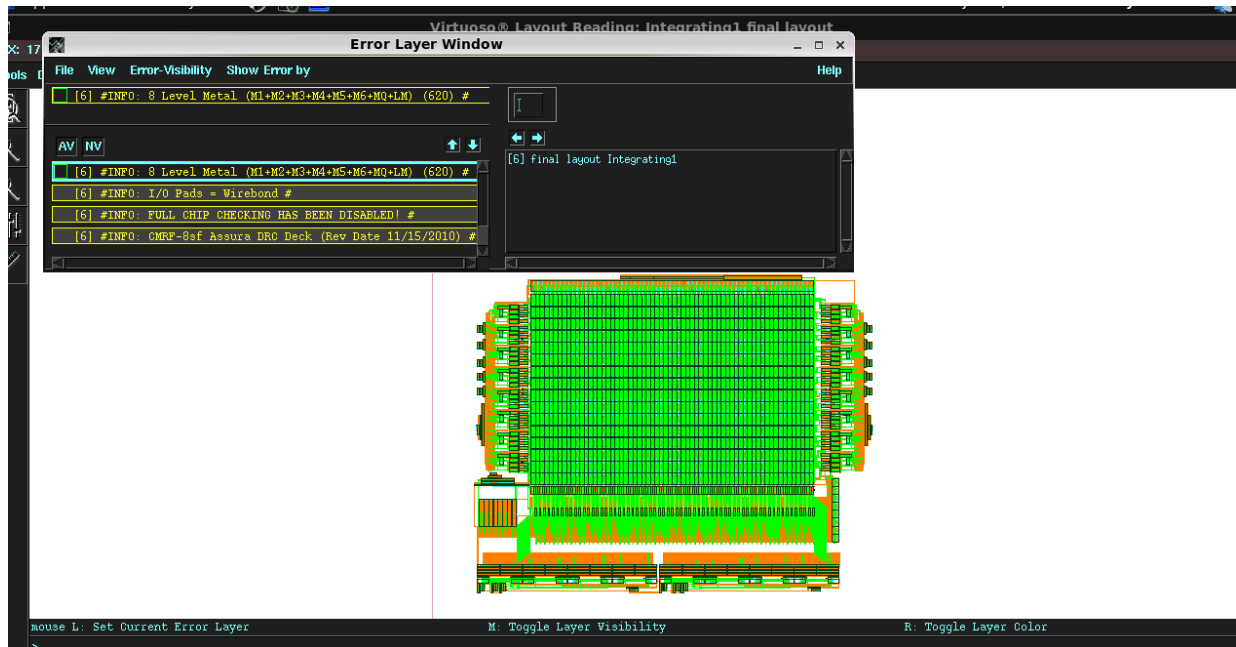


Fig.24 DRC Report

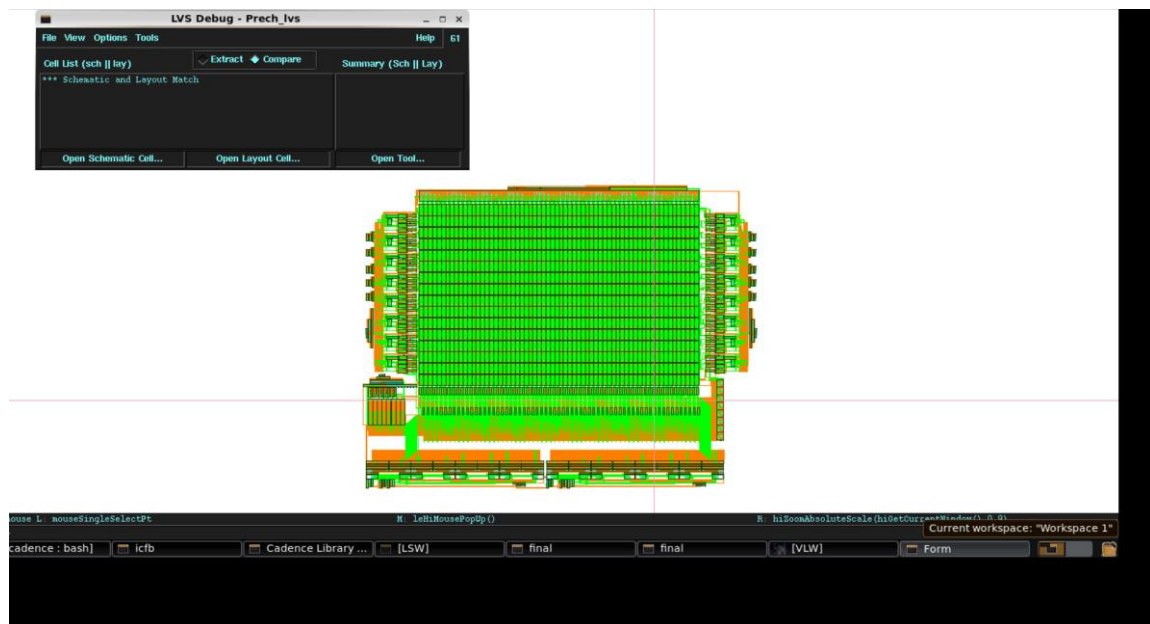


Fig.25 LVS Report

8. TIMING ANALYSIS

8.1 Hspice Code

```
$
$
$transistor model

.include "/home/cad/kits/IBM_CMRF8SF-
LM013/IBM_PDK/cmrf8sf/V1.2.0.0LM/HSPICE/models/model013.lib_inc"

.include "working.sp"

.option post runlvl=5

xi addr0 addr1 addr2 addr3 addr4 addr5 addr6 addr7 addr_en addr_en1
+ baddr0 baddr1 baddr2 baddr3 baddr4 baddr5 baddr6 baddr7 clk in_data0 in_data1
+ in_data2 in_data3 in_data4 in_data5 in_data6 in_data7 out_data0 out_data1
+ out_data2 out_data3 out_data4 out_data5 out_data6 out_data7 read_en1 read_en2
+ ref wr NEW

vdd vdd! gnd! 1.2V
Vref ref gnd! 0.6V
Cout_1 out_data0 0 25fF
Cout_2 out_data1 0 25fF
Cout_3 out_data2 0 25fF
Cout_4 out_data3 0 25fF
Cout_5 out_data4 0 25fF
Cout_6 out_data5 0 25fF
Cout_7 out_data6 0 25fF
Cout_8 out_data7 0 25fF

*****Address lines for row and column decoders1

Va0 addr0 gnd! PWL 0ns 1.2V
Va1 addr1 gnd! PWL 0ns 1.2V
Va2 addr2 gnd! PWL 0ns 1.2V
Va3 addr3 gnd! PWL 0ns 1.2V
Va4 addr4 gnd! PWL 0ns 1.2V
Va5 addr5 gnd! PWL 0ns 1.2V
Va6 addr6 gnd! PWL 0ns 1.2V
Va7 addr7 gnd! PWL 0ns 1.2V

*****Address lines for row and column decoders2
```

```

Vb0 baddr0 gnd! PWL 0ns 1.2V
Vb1 baddr1 gnd! PWL 0ns 1.2V
Vb2 baddr2 gnd! PWL 0ns 1.2V
Vb3 baddr3 gnd! PWL 0ns 1.2V
Vb4 baddr4 gnd! PWL 0ns 1.2V
Vb5 baddr5 gnd! PWL 0ns 1.2V
Vb6 baddr6 gnd! PWL 0ns 1.2V
Vb7 baddr7 gnd! PWL 0ns 1.2V

```

*****Data values to be written

```

Vd1 in_data0 gnd! PWL (0ns 1.2V 125ns 1.2V 125.2ns 0V)
Vd2 in_data1 gnd! PWL (0ns 0V 125ns 0V 125.2ns 1.2V)
Vd3 in_data2 gnd! PWL (0ns 1.2V 125ns 1.2V 125.2ns 0V)
Vd4 in_data3 gnd! PWL (0ns 0V 125ns 0V 125.2ns 1.2V)
Vd5 in_data4 gnd! PWL (0ns 1.2V 125ns 1.2V 125.2ns 0V)
Vd6 in_data5 gnd! PWL (0ns 0V 125ns 0V 125.2ns 1.2V)
Vd7 in_data6 gnd! PWL (0ns 1.2V 125ns 1.2V 125.2ns 0V)
Vd8 in_data7 gnd! PWL (0ns 0V 125ns 0V 125.2ns 1.2V)

```

*****Values for Read enable, Write enable and CLK

```

V1 wr gnd! PWL (0ns 0V 50ns 0V 50.2ns 1.2V 60ns 1.2V 60.2ns 0V 150ns 0V 150.2ns 1.2V 160ns
1.2V 160.2ns 0V)
V2 addr_en gnd! PWL (0ns 0V 50ns 0V 50.2ns 1.2V 70ns 1.2V 70.2ns 0V 150ns 0V 150.2ns 1.2V 170ns
1.2V 170.2ns 0V)
V3 addr_en1 gnd! PWL (0ns 0V 80ns 0V 80.2ns 1.2V 100ns 1.2V 100.2ns 0V 180ns 0V 180.2ns 1.2V
200ns 1.2V 200.2ns 0V)
V4 read_en1 gnd! PWL (0ns 0V 80ns 0V 80.2ns 1.2V 100ns 1.2V 100.2ns 0V 180ns 0V 180.2ns 1.2V
200ns 1.2V 200.2ns 0V)
V5 read_en2 gnd! PWL (0ns 0V 50ns 0V 50.2ns 1.2V 70ns 1.2V 70.2ns 0V 150ns 0V 150.2ns 1.2V
170ns 1.2V 170.2ns 0V)
V6 clk gnd! PWL(0ns 0V 50ns 0V 50.2ns 1.2V 100ns 1.2V 100.2ns 0V 150ns 0V 150.2ns 1.2V 200ns
1.2V 200.2ns 0V 250ns 0V 250.2ns 1.2V 300ns 1.2V 300.2ns 0V)

```

```

.tr 0.01ns 500ns

```

```

.end

```

8.2 Testing the correct functionality:

To check the correct functionality, writing and reading of word 10101010 is checked.

 


Fig.26 Functionality check of write 10101010

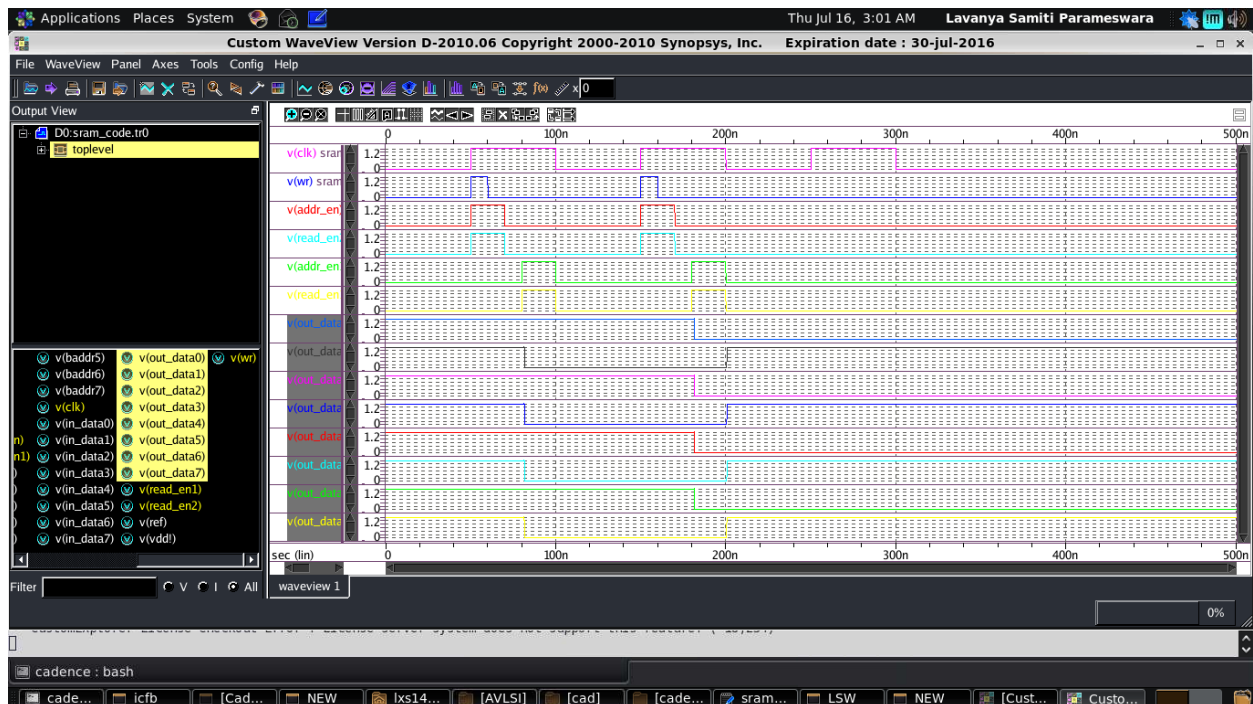


Fig.27 Functionality check of read 10101010

8.3 Worst case writing time for '0' = 451 ps and for '1' = 467 ps

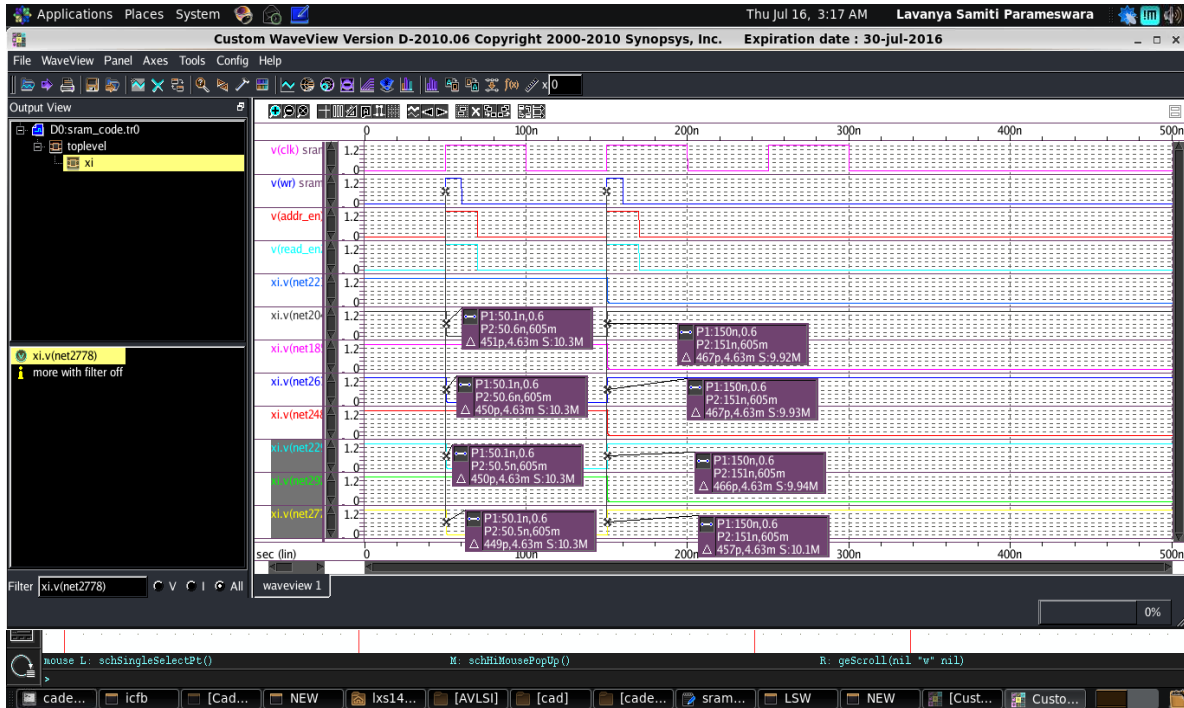


Fig.28 Worst Case Write Time for Zero and One

8.4 Worst case reading time for '0' = 20.6 ns and for '1' = 1.59ns

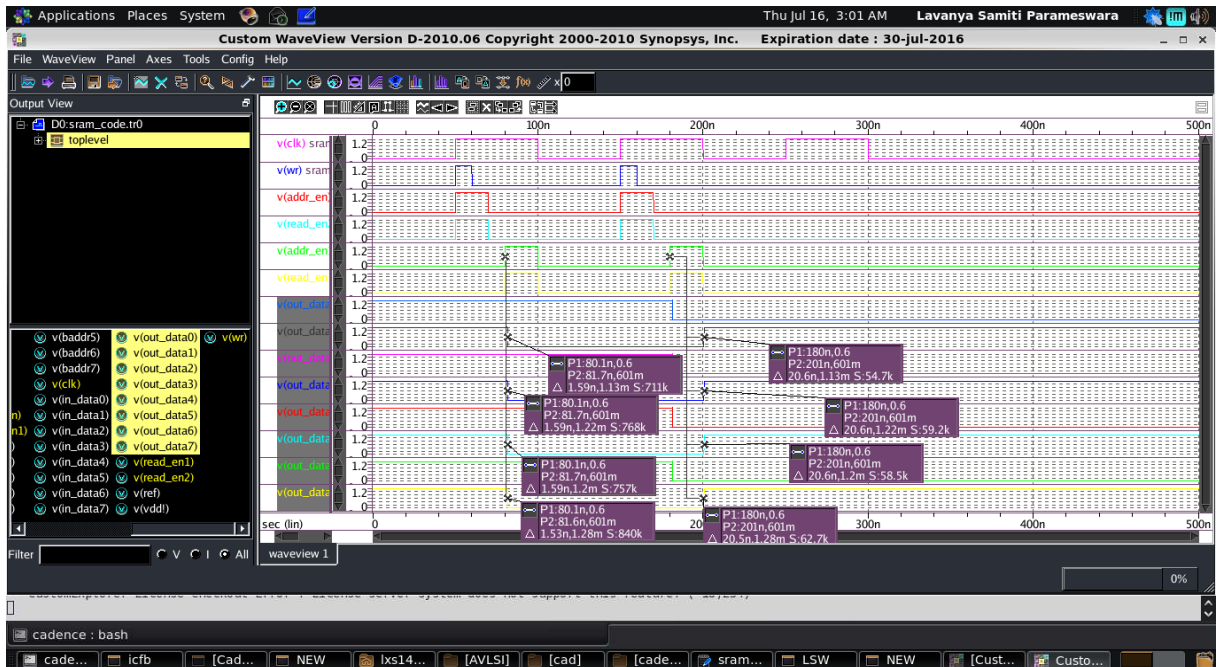


Fig.29 Worst Case Read Time for Zero and One

8.5 Operating Frequency = 1GHz

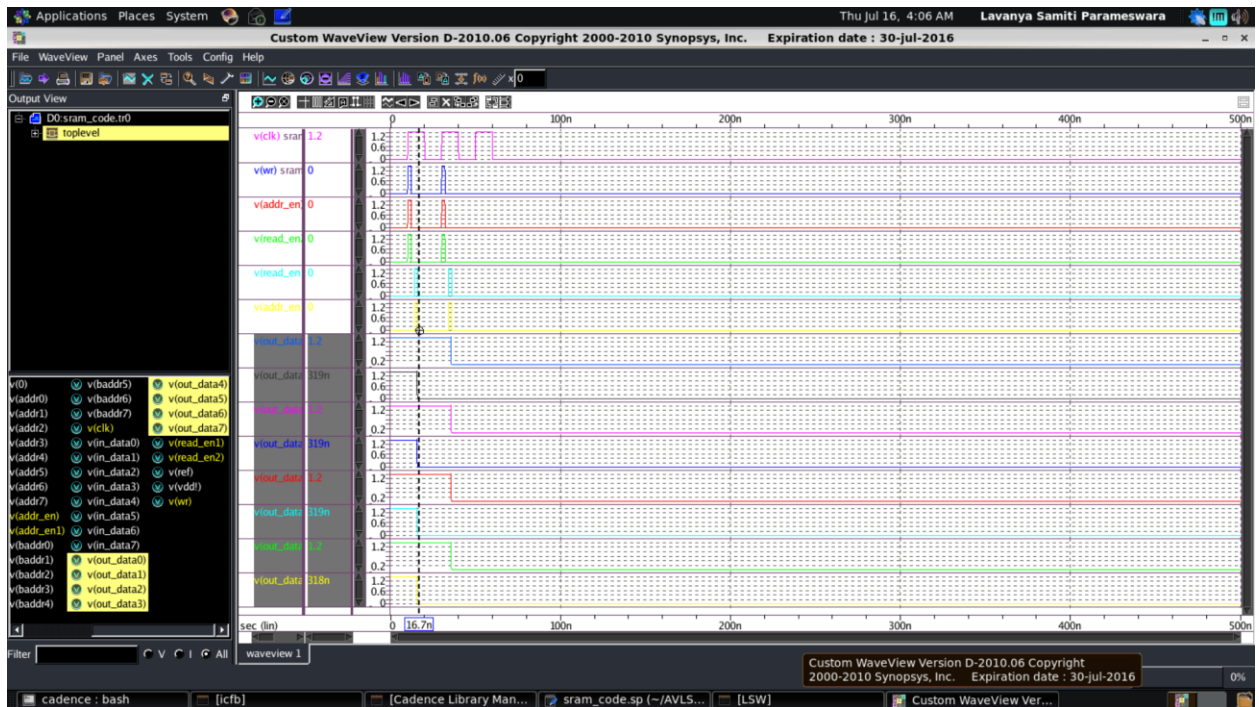


Fig. 30 Operating frequency

9. RESULTS AND CONCLUSIONS

A 256 word SRAM was designed with an area of 36347.723 sq um.

The Worst Case Read and Write Times are found to be 20.6 ns and 467 ps.

The operating frequency is 1GHz.

